
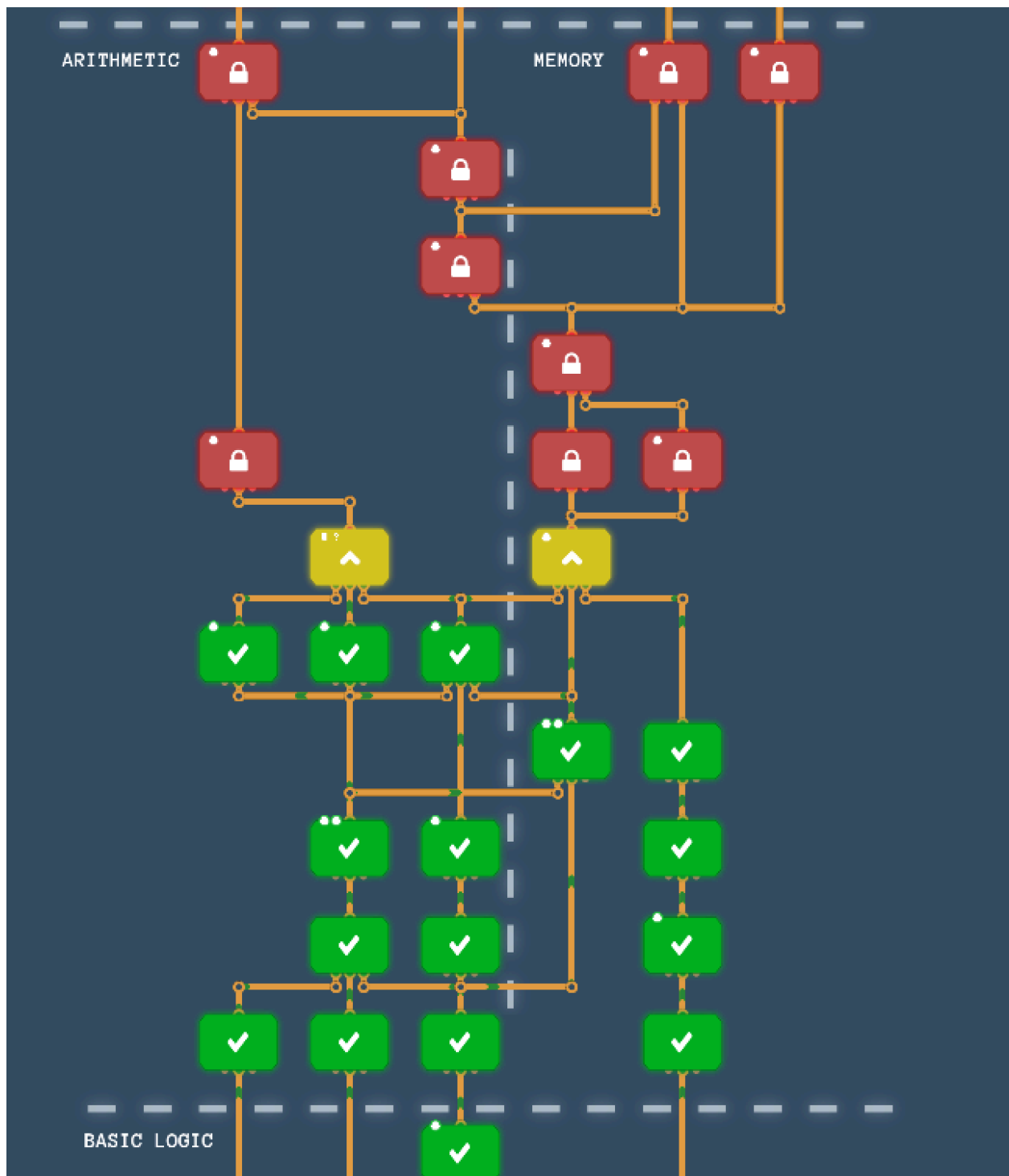


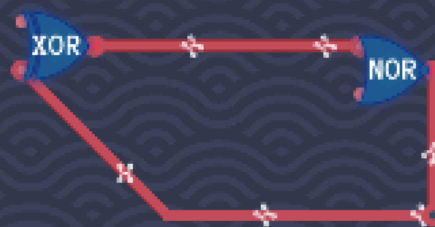March 30th updates: I finished some on the Arithmetics and Memory part of the game.




CIRCULAR DEPENDENCY





ODD NUMBER OF SIGNALS






DOUBLE TROUBLE

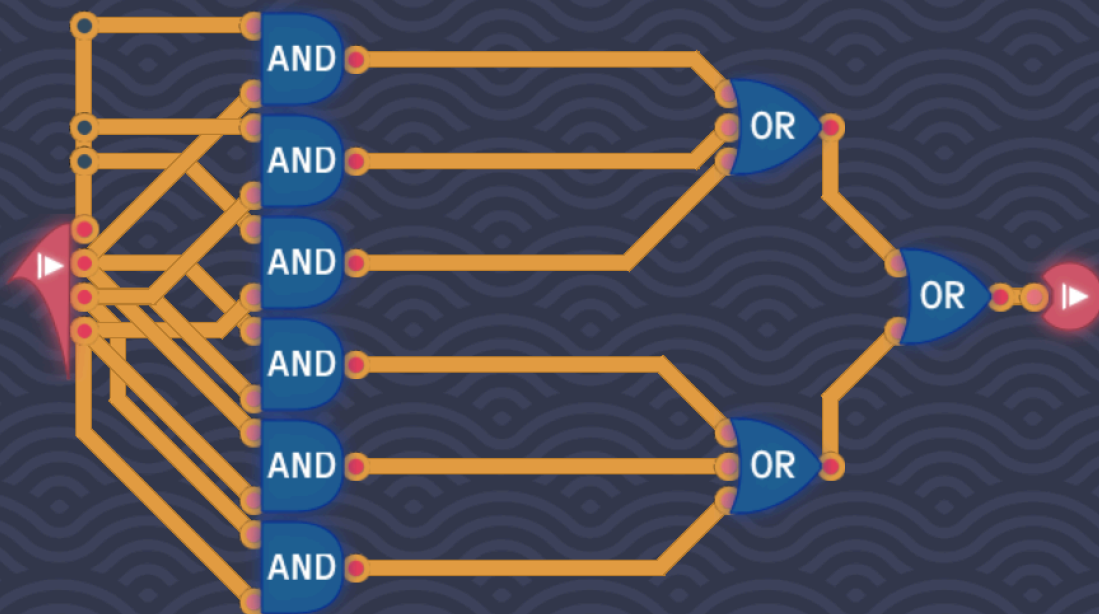

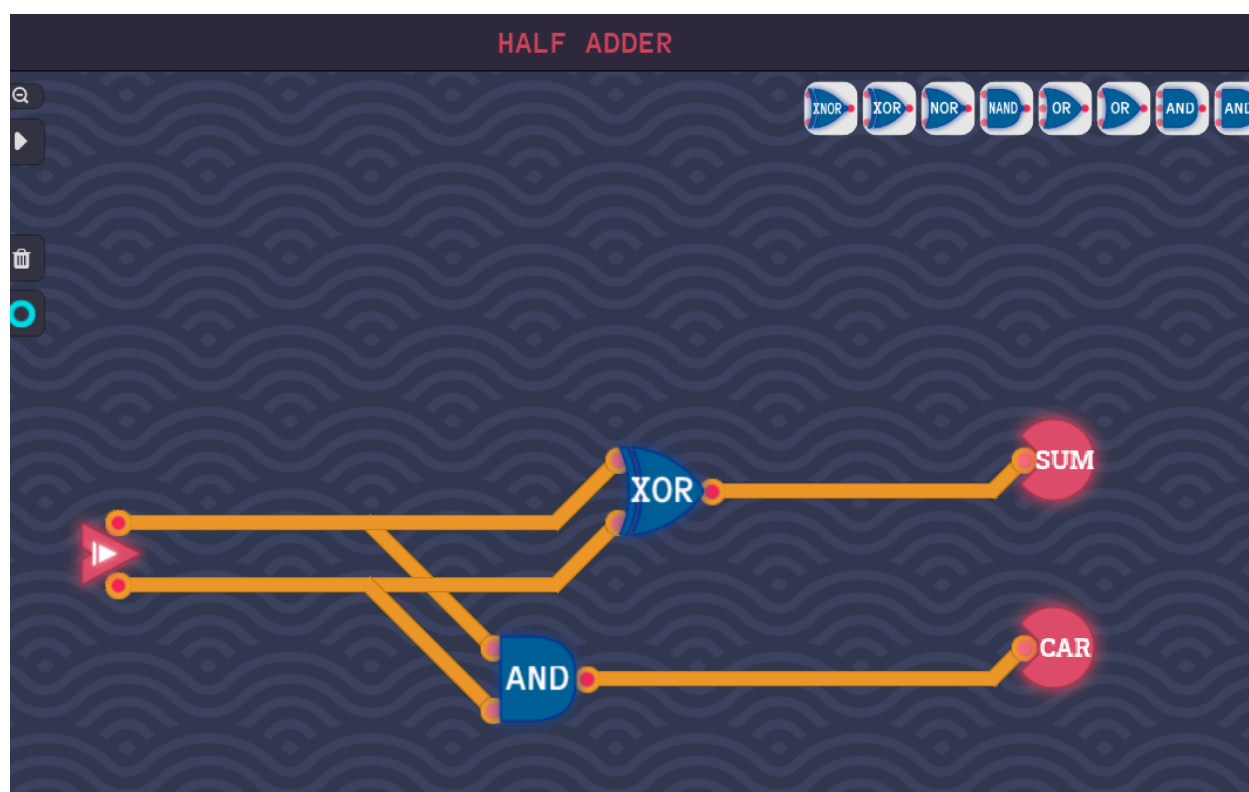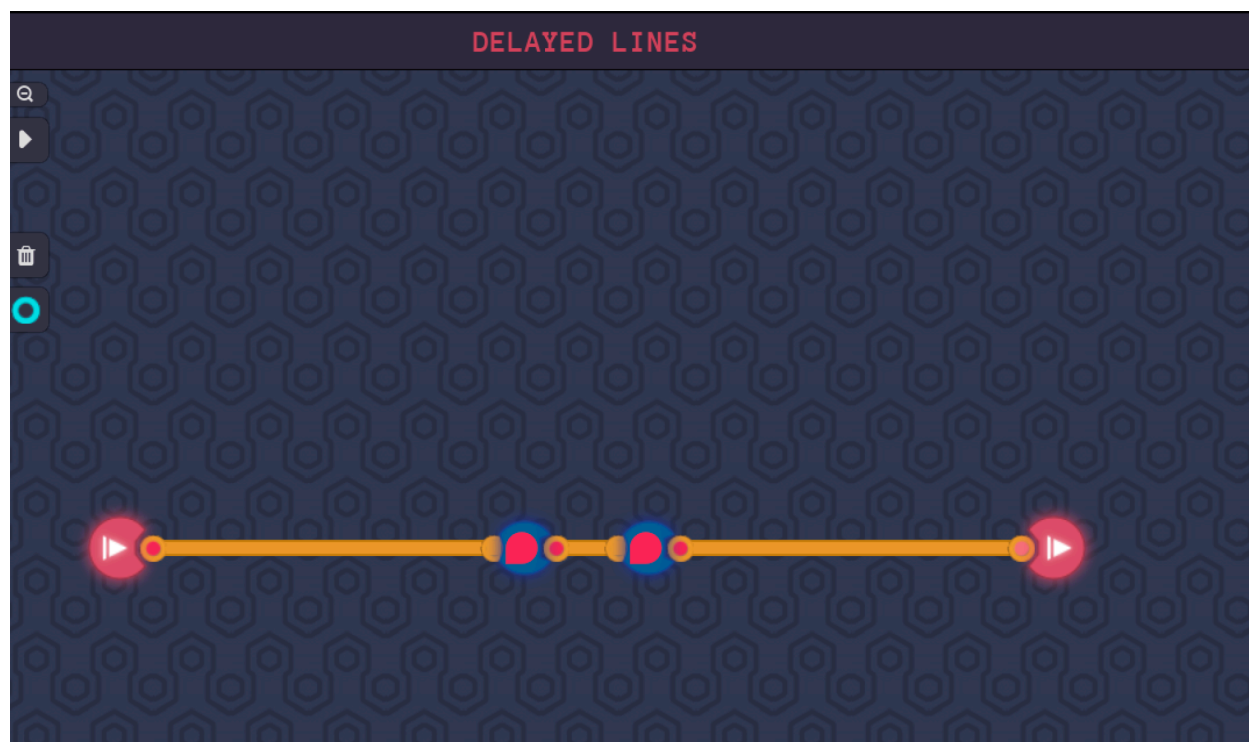


COUNTING SIGNALS

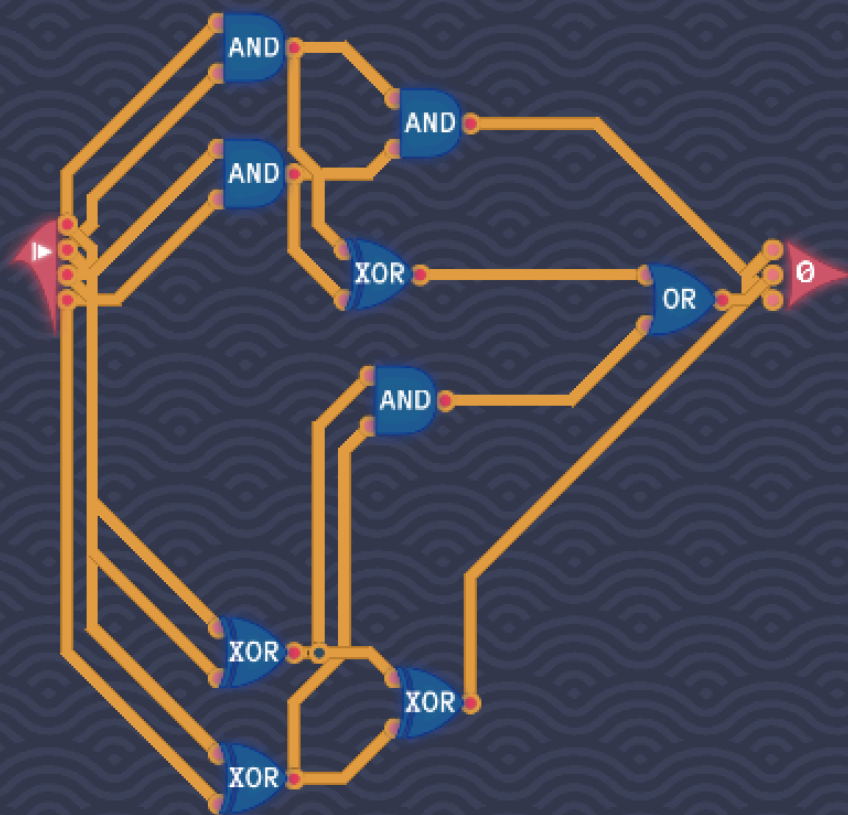


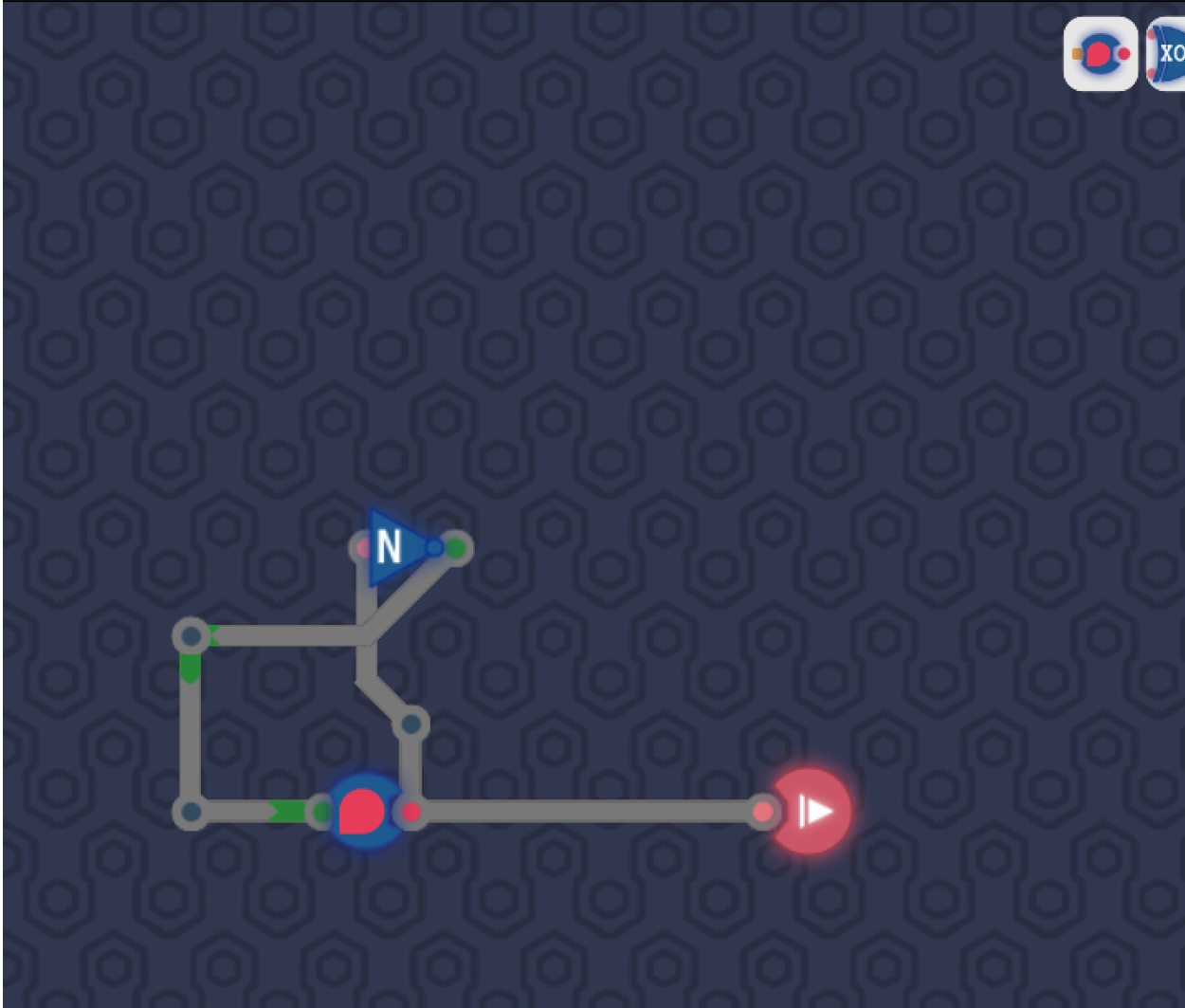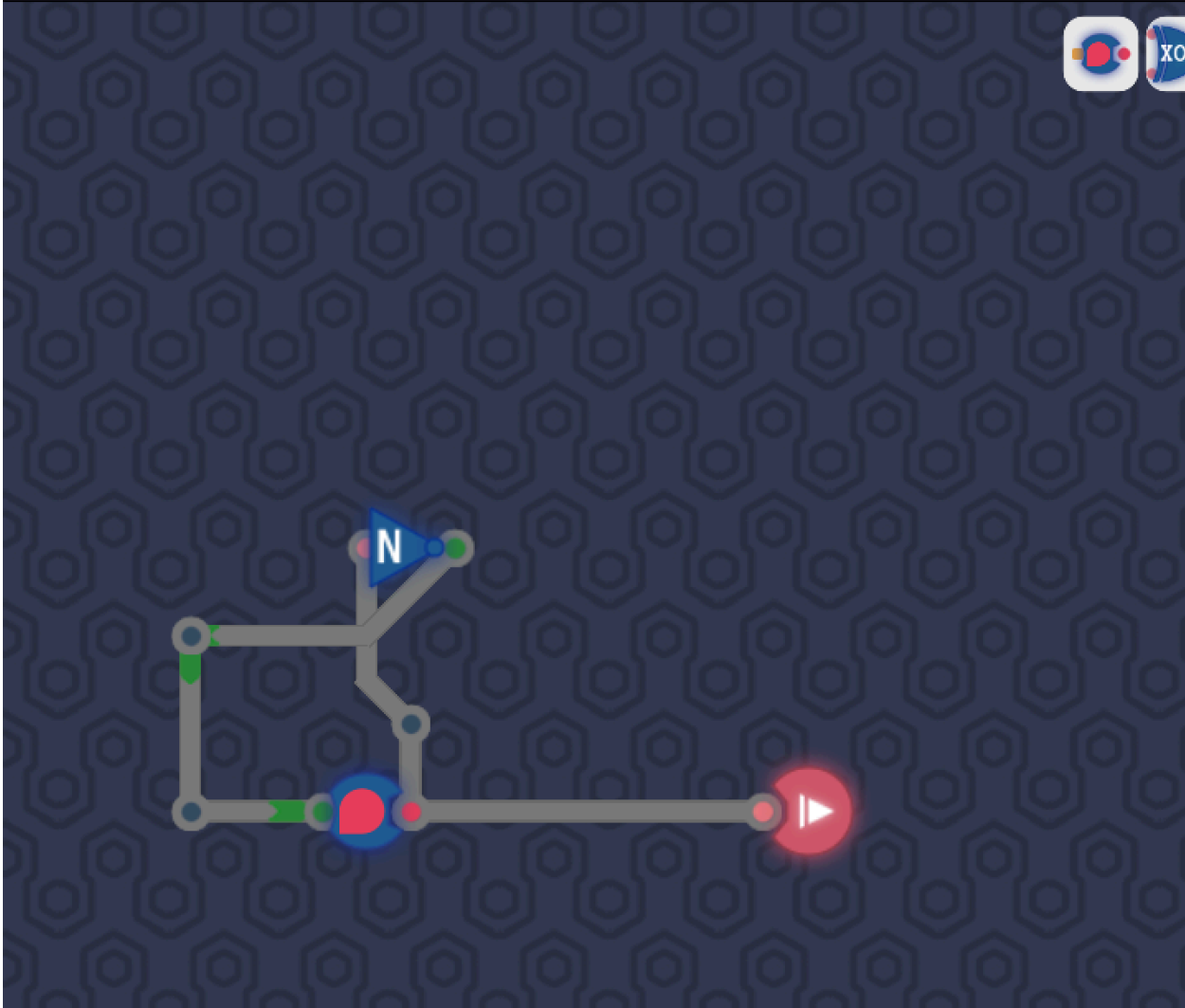


FULL ADDER

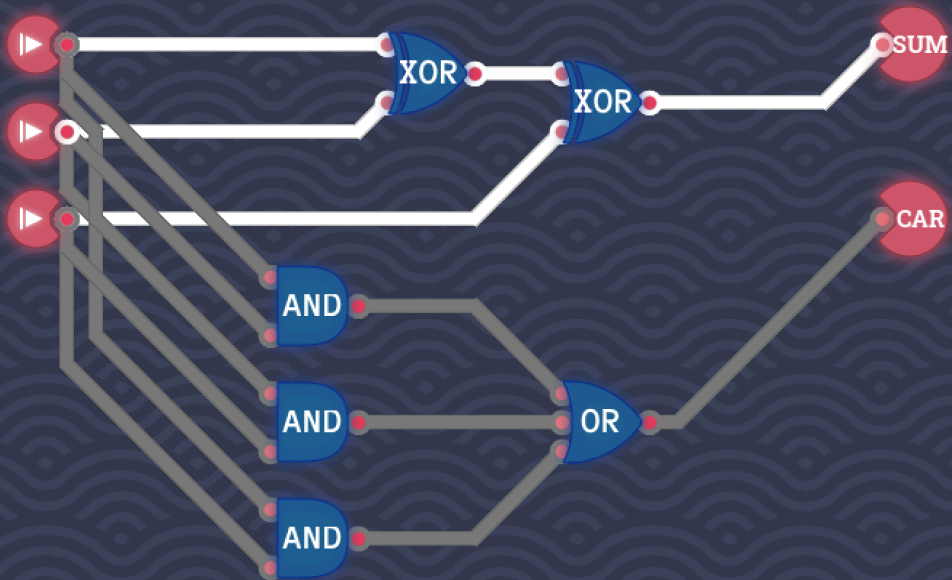


DOUBLE THE NUMBER

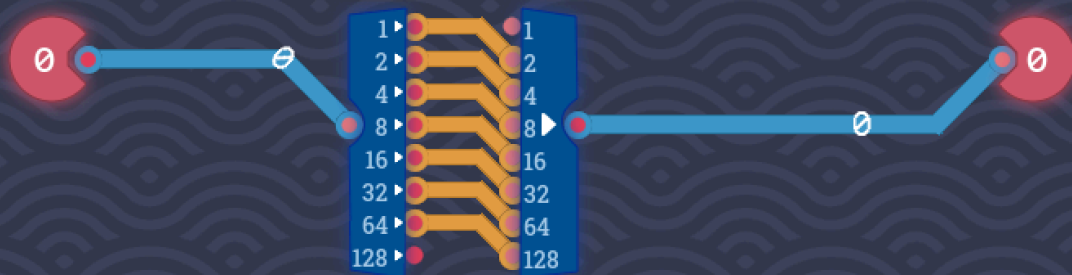


BIT INVERTER

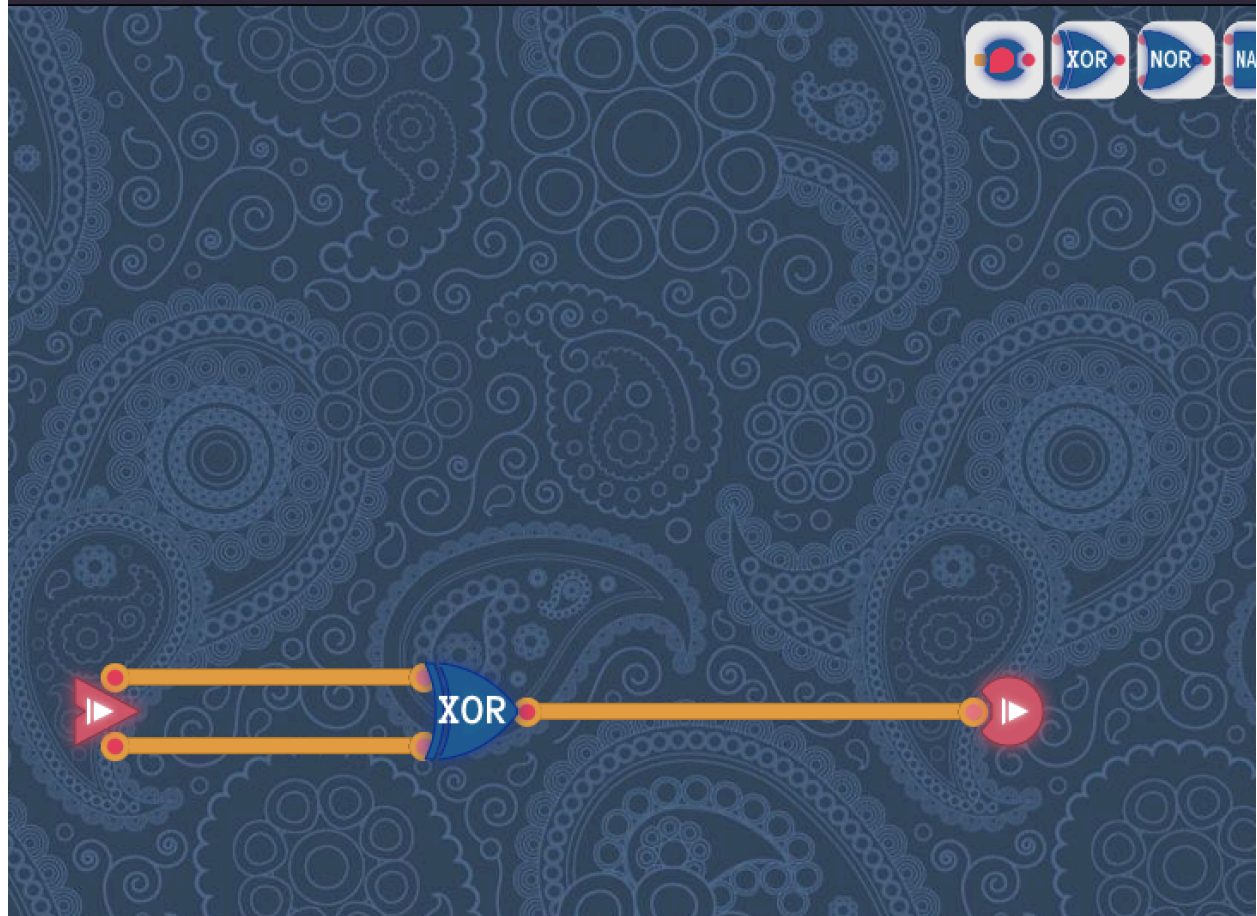


BIT SWITCH

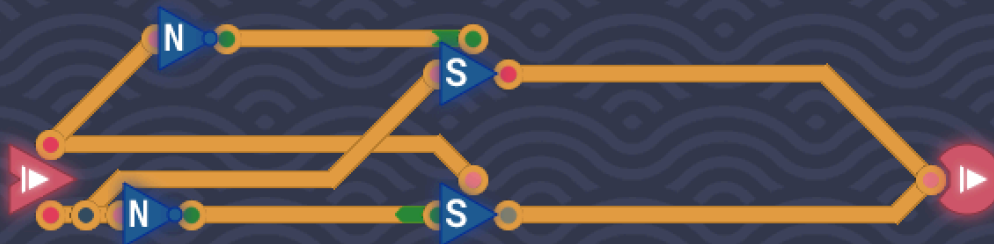

ADDING BYTES

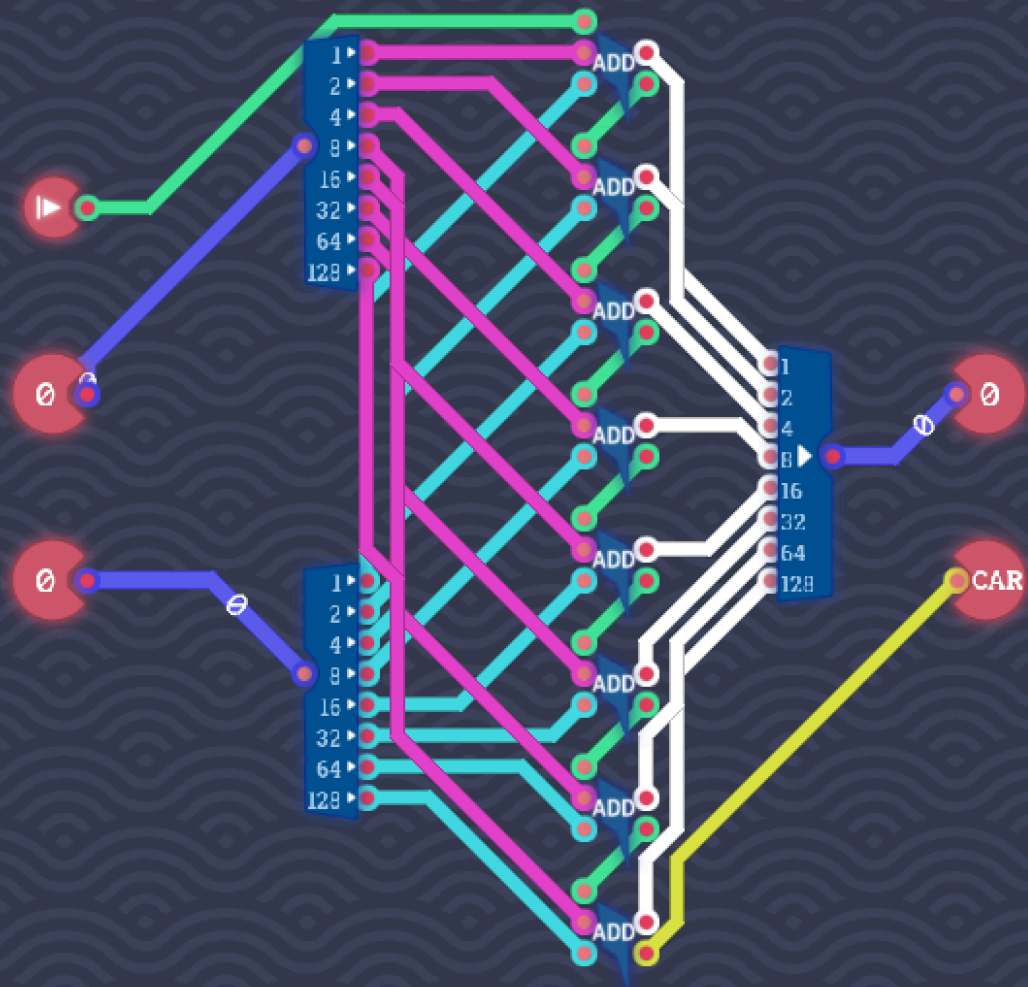

BYTE NOT

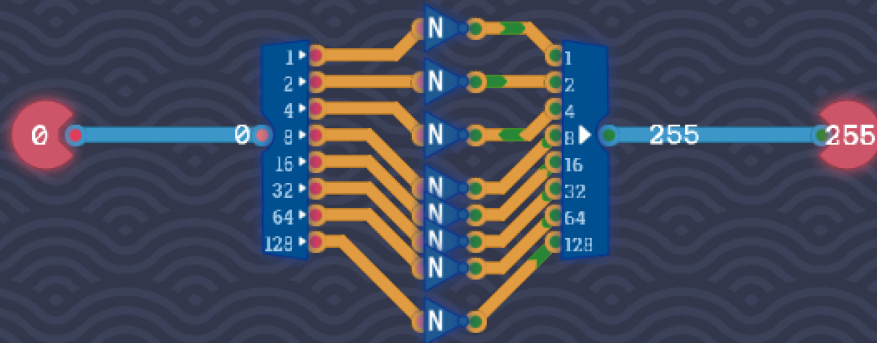

BYTE OR

